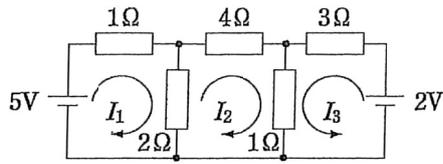


第1章 ワークシート解答

1. (1)



$$\begin{aligned} 3I_1 - 2I_2 + 0 &= 5 \\ -2I_1 + 7I_2 + I_3 &= 0 \\ 0 + I_2 + 4I_3 &= 2 \end{aligned} \rightarrow \begin{bmatrix} 3 & -2 & 0 \\ -2 & 7 & 1 \\ 0 & 1 & 4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 2 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 3 & -2 & 0 \\ -2 & 7 & 1 \\ 0 & 1 & 4 \end{vmatrix} = 84 - 3 - 16 = 65$$

$$I_1 = \frac{\begin{vmatrix} 5 & -2 & 0 \\ 0 & 7 & 1 \\ 2 & 1 & 4 \end{vmatrix}}{\Delta} = \frac{140 - 4 - 5}{65} = \frac{131}{65}$$

$$I_2 = \frac{\begin{vmatrix} 3 & 5 & 0 \\ -2 & 0 & 1 \\ 0 & 2 & 4 \end{vmatrix}}{\Delta} = \frac{-6 - (-40)}{65} = \frac{34}{65}$$

$$I_3 = \frac{\begin{vmatrix} 3 & -2 & 5 \\ -2 & 7 & 0 \\ 0 & 1 & 2 \end{vmatrix}}{\Delta} = \frac{42 - 10 - 8}{65} = \frac{24}{65}$$

$$I_{R1(1\Omega)} = I_1 = \frac{131}{65} = 2.02 \text{ A} \quad (\text{答}) \quad 2.02 \text{ A, 右向き}$$




$$I_{R2(4\Omega)} = I_2 = \frac{34}{65} = 0.523 \text{ A} \quad (\text{答}) \quad 0.523 \text{ A, 右向き}$$

$$I_{R3(3\Omega)} = I_3 = \frac{24}{65} = 0.369 \text{ A} \quad (\text{答}) \quad 0.369 \text{ A, 左向き}$$

$$I_{R4(1\Omega)} = I_1 - I_2 = \frac{97}{65} = 1.49 \text{ A} \quad (\text{答}) \quad 1.49 \text{ A, 下向き}$$

$$I_{R5(1\Omega)} = I_2 + I_3 = \frac{34}{65} + \frac{24}{65} = \frac{58}{65} = 0.892 \text{ A} \quad (\text{答}) \quad 0.892 \text{ A, 下向き}$$

(2)

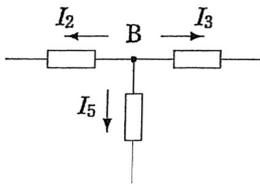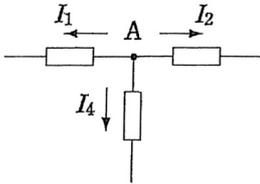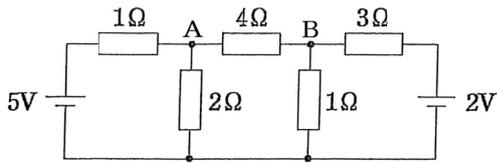

$$\text{A点: } \frac{V_A - 5}{1} + \frac{V_A}{2} + \frac{V_A - V_B}{4} = 0 \rightarrow 7V_A - V_B = 20 \quad \cdots \textcircled{1}$$

$$\text{B点: } \frac{V_B - V_A}{4} + \frac{V_B}{1} + \frac{V_B - 2}{3} = 0 \rightarrow -3V_A + 19V_B = 8 \quad \cdots \textcircled{2}$$

①, ②より

$$V_B = 7V_A - 20$$

$$-3V_A + 133V_A - 380 = 8$$

$$130V_A = 388$$

$$V_A = \frac{388}{130} = \frac{194}{65}$$

$$V_B = \frac{58}{65}$$

$$I_{R1(1\Omega)} = I_1 = \frac{V_A - 5}{R_1} = \frac{194}{65} - \frac{325}{65} = -\frac{131}{65} = -2.02 \text{ A} \quad (\text{答}) \quad 2.02 \text{ A, 右向き}$$



$$I_{R2(4\Omega)} = \frac{V_A - V_B}{R_2} = \frac{\frac{194}{65} - \frac{58}{65}}{4} = \frac{1}{4} \times \frac{136}{65} = \frac{34}{65} = 0.523 \text{ A} \quad (\text{答}) \quad 0.523 \text{ A, 右向き}$$

$$I_{R4(2\Omega)} = \frac{V_A}{R_4} = \frac{1}{2} \times \frac{194}{65} = \frac{97}{65} = 1.49 \text{ A} \quad (\text{答}) \quad 1.49 \text{ A, 下向き}$$

$$I_{R3(3\Omega)} = \frac{V_B - 2}{R_3} = \frac{\frac{58}{65} - 2}{3} = \frac{1}{3} \times \frac{58 - 130}{65} = -\frac{24}{65} = -0.369 \text{ A} \quad (\text{答}) \quad 0.369 \text{ A, 左向き}$$

$$I_{R5(1\Omega)} = \frac{V_B}{R_5} = \frac{58}{65} = 0.892 \text{ A} \quad (\text{答}) \quad 0.892 \text{ A, 下向き}$$

(3)

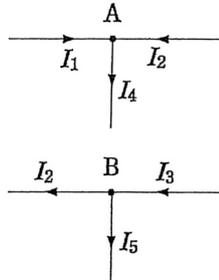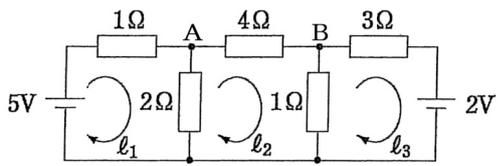

A点

$$I_1 + I_2 = I_4 \quad \cdots \textcircled{1}$$

$$I_1 + 2I_4 = 5 \quad \cdots \textcircled{2}$$

B点

$$I_3 = I_2 + I_5 \quad \cdots \textcircled{3}$$

$$3I_3 + I_5 = 2 \quad \cdots \textcircled{4}$$

AB間

$$-4I_2 + I_5 - 2I_4 = 0 \quad \cdots \textcircled{5}$$

①②より

$$I_1 = I_4 - I_2$$

$$I_4 - I_2 + 2I_4 = -I_2 + 3I_4 = 5 \quad \cdots \textcircled{6}$$

③④より

$$I_5 = I_3 - I_2$$

$$3I_3 + I_3 - I_2 = 4I_3 - I_2 = 2 \quad \cdots \textcircled{7}$$

③⑤より

$$I_5 = I_3 - I_2$$

$$-4I_2 + I_3 - I_2 - 2I_4 = -5I_2 + I_3 - 2I_4 = 0 \quad \cdots \textcircled{8}$$

⑦⑧より

$$I_3 = 5I_2 + 2I_4$$

$$4(5I_2 + 2I_4) - I_2 = 20I_2 + 8I_4 - I_2 = 19I_2 + 8I_4 = 2 \quad \cdots \textcircled{9}$$

⑥⑨より

$$I_2 = 3I_4 - 5$$

$$19(3I_4 - 5) + 8I_4 = 57I_4 - 95 + 8I_4 = 2$$

したがって, $65I_4 = 97 \rightarrow I_{4(2\Omega)} = \frac{97}{65} = 1.49 \text{ A}$ (答) 1.49 A, 下向き


$$I_{2(4\Omega)} = 3I_4 - 5 = 3 \times \frac{97}{65} - 5 = -\frac{34}{65} = -0.523 \text{ A} \quad (\text{答}) \quad 0.523 \text{ A, 右向き}$$

$$I_{3(3\Omega)} = 5I_2 + 2I_4 = 5 \times \left(-\frac{34}{65}\right) + 2 \times \frac{97}{65} = \frac{24}{65} = 0.369 \text{ A} \quad (\text{答}) \quad 0.369 \text{ A, 左向き}$$

$$I_{5(1\Omega)} = I_3 - I_2 = \frac{24}{65} - \left(-\frac{34}{65}\right) = \frac{58}{65} = 0.892 \text{ A} \quad (\text{答}) \quad 0.892 \text{ A, 下向き}$$

$$I_{1(1\Omega)} = I_4 - I_2 = \frac{97}{65} - \left(-\frac{34}{65}\right) = \frac{131}{65} = 2.02 \text{ A} \quad (\text{答}) \quad 2.02 \text{ A, 右向き}$$

2.

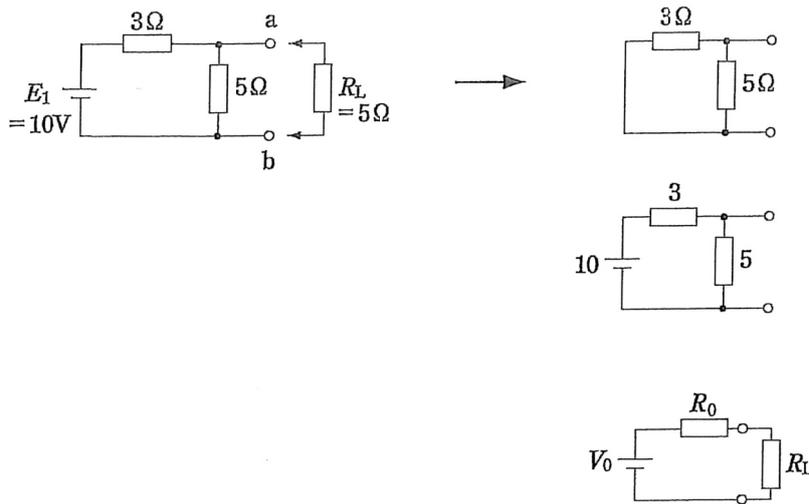


$$R_0 = \frac{3 \times 5}{3 + 5} = \frac{15}{8} \Omega$$

$$V_0 = \frac{5}{3 + 5} \times 10 = \frac{50}{8} \text{ V}$$

したがって,

$$I_{R_L} = \frac{V_0}{R_0 + R_L} = \frac{\frac{50}{8}}{\frac{15}{8} + 5} = \frac{50}{55} = 0.909 \text{ A} \quad (\text{答}) \quad 0.909 \text{ A}$$

3. (1)

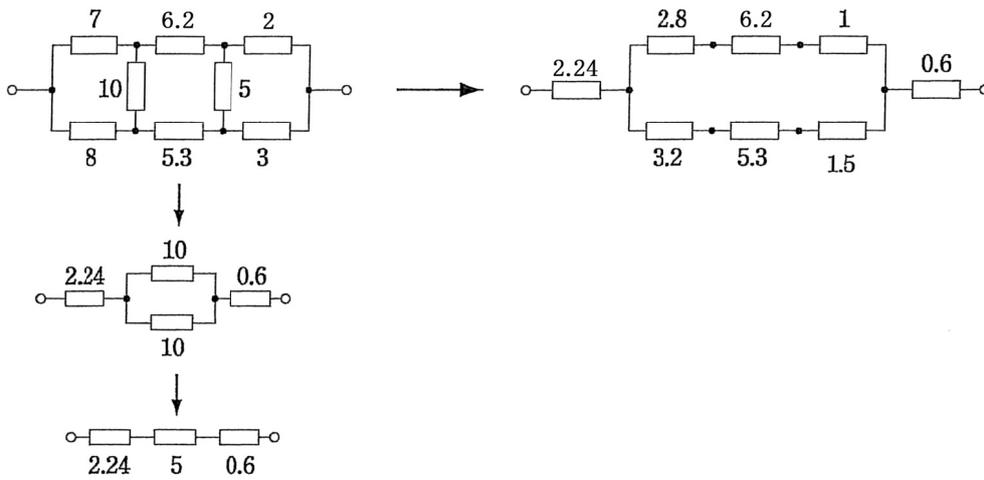

$$R_1 = \frac{7 \times 8}{7 + 8 + 10} = \frac{56}{25} = 2.24 \Omega$$

$$R_2 = \frac{7 \times 10}{25} = \frac{70}{25} = 2.8 \Omega$$

$$R_3 = \frac{8 \times 10}{25} = \frac{80}{25} = 3.2 \Omega$$


$$R_4 = \frac{2 \times 3}{5 + 2 + 3} = \frac{6}{10} = 0.6 \Omega$$

$$R_5 = \frac{5 \times 3}{10} = \frac{15}{10} = 1.5 \Omega$$

$$R_6 = \frac{5 \times 2}{10} = \frac{10}{10} = 1 \Omega$$

$$R_0 = 7.84 \Omega \quad (\text{答}) \quad 7.84 \Omega$$

(2)

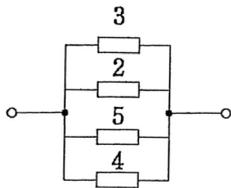

$$R = \frac{1}{\frac{1}{3} + \frac{1}{2} + \frac{1}{5} + \frac{1}{4}} = \frac{60}{20 + 30 + 12 + 15} = \frac{60}{77} = 0.779 \Omega \quad (\text{答}) \quad 0.779 \Omega$$

4.

$$I_R = \frac{r}{r+R} I$$

$$R_R = R I_R^2 = R \frac{r^2}{(r+R)^2} I^2 \quad (\text{答})$$

電力 P_R が最大となる条件は $\frac{dP_R}{dR} = 0$ より

$$\begin{aligned} \frac{dP_R}{dR} &= \frac{d}{dR} \left\{ r^2 I^2 \frac{R}{(r+R)^2} \right\} \\ &= r^2 I^2 \left\{ \frac{(r+R)^2 - 2R(r+R)}{(r+R)^4} \right\} \\ &= r^2 I^2 \frac{r+R-2R}{(r+R)^3} = r^2 I^2 \frac{r-R}{(r+R)^3} = 0 \end{aligned}$$

したがって、 $R = r$ のとき P_R が最大

$$\begin{aligned} P_{R \max} &= r \frac{r^2}{(r+r)^2} I^2 \\ &= \frac{r^3}{(2r)^2} I^2 \\ &= \frac{r}{4} I^2 \quad (\text{答}) \end{aligned}$$

5. (1) 証明は、1-4-1項を参照。

(2) 式1-63より $R_2 R_3 = R_1 R_4$ となるから

$$2 \times 5 = 10 \times R_4$$

$$R_4 = 1$$

したがって、 $R_4 = 1\Omega$ (答)